

Template Week 2 – Logic

Student number:

582122

Assignment 2.1: Parking lot

Which gates do you need?

-I will need an AND gate because the whole parking lot is only full when all individual lots are full at the same time.

Parking lot 1	Parking lot 2	Parking lot 3	Result (full)
0	0	0	0
0	0	1	0
0	1	0	0
0	0	1	0
1	0	0	0
1	1	0	0
1	0	1	0
1	1	1	1

Assignment 2.2: Android or iPhone

Which gates do you need?

XOR

Android phone	iPhone	Result (Phone in possession)
0	0	0
1	0	1
0	1	1
1	1	0

Assignment 2.3: Four NAND gates

A	B	Q
0	0	1


0	1	1
1	0	1
1	1	0

How can the design be simplified?

Assignment 2.4: Getting to know Logisim evolution


Screenshot of the design with your name and student number in it:

viktoriakrastanova582122

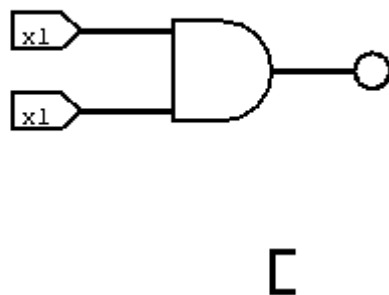


Assignment 2.5: SR Latch

Screenshot SR Latch in Logisim with your name and student number:

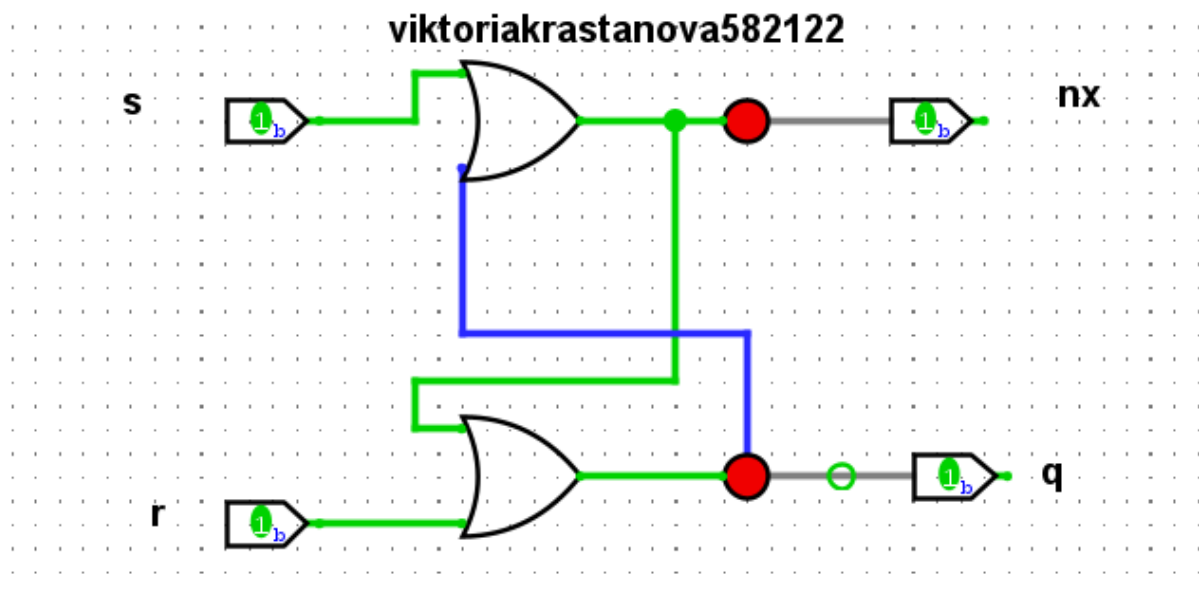

Assignment 2.6: Vending Machine

Screenshot Vending Machine in Logisim with your name and student number:

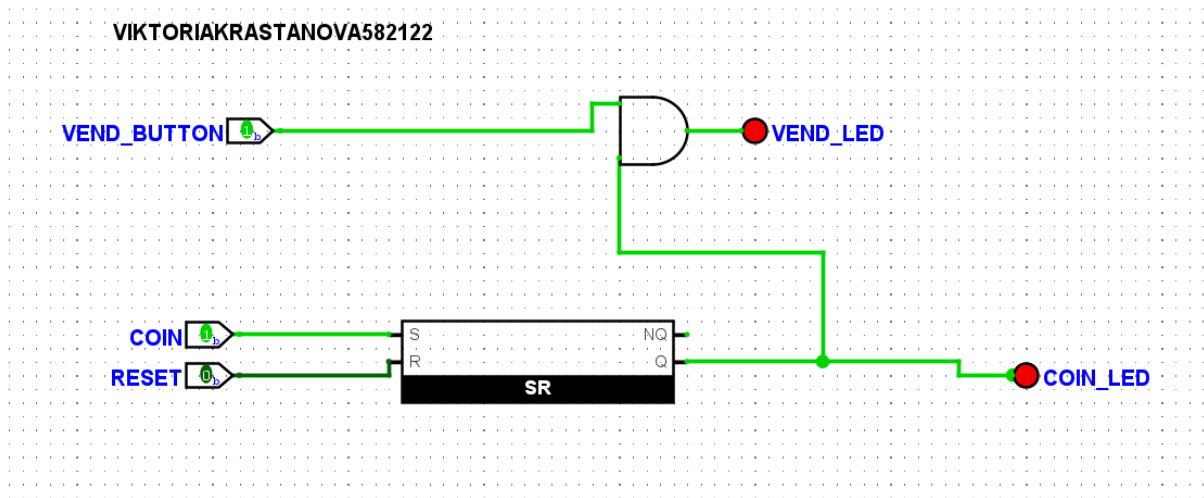

Assignment 2.7: Bitwise operators

Complete the java source code for bitwise operators. Put the source code here.

```
import java.util.Scanner;
```

```
public class Main {  
    public static void main(String[] args) {  
        System.out.println("1. Check if number is odd");  
        System.out.println("2. Check if number is a power of 2");  
        System.out.println("3. Check two's complement of a number");  
        System.out.println("Choose an operation: ");  
  
        Scanner scanner = new Scanner(System.in);  
        int choice = scanner.nextInt();  
        int num;  
  
        switch (choice) {  
            case 1:  
                System.out.println("Choose a number: ");  
                num = scanner.nextInt();  
                numIsOdd(num);  
                break;  
  
            case 2:  
                System.out.println("Choose a number: ");  
                num = scanner.nextInt();  
                numIsPowerOf2(num);  
                break;  
  
            case 3:  
                System.out.println("Choose a number: ");  
                num = scanner.nextInt();  
                numIsTwoComplement(num);  
                break;  
        }  
    }  
}
```

```

        break;

    case 3:
        System.out.println("Choose a number: ");
        num = scanner.nextInt();
        twosComplement(num);
        break;
    }
}

public static void numIsOdd(int num) {
    if (num % 2 == 0) {
        System.out.println("The number " + num + " is not odd!");
    } else {
        System.out.println("The number " + num + " is odd!");
    }
}

public static void numIsPowerOf2(int num) {
    if ((num & num - 1) == 0) {
        System.out.println("The number " + num + " is a power of 2!");
    } else {
        System.out.println("The number " + num + " is not a power of 2!");
    }
}

public static void twosComplement(int num) {
    num = ~num;
    System.out.println("This is the negative version of your number: " + (num + 1));
    num = ~num;
    System.out.println("And now it's back to a positive: " + num);
}
}

```

Assignment 2.8: Java Application Bit Calculations

Create a java program that accepts user input and presents a menu with options.

1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number?

Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

Keep this application because you need to expand it in week 6 for calculating network segments.

Paste source code here, with a screenshot of a working application.

```
1. Check if number is odd
2. Check if number is a power of 2
3. Check two's complement of a number
Choose an operation:
3
Choose a number:
651
This is the negative version of your number: -651
And now it's back to a positive: 651

Process finished with exit code 0
```

```
1. Check if number is odd
2. Check if number is a power of 2
3. Check two's complement of a number
Choose an operation:
2
Choose a number:
6581486
The number 6581486 is not a power of 2!

Process finished with exit code 0
```

```
1. Check if number is odd
2. Check if number is a power of 2
3. Check two's complement of a number
Choose an operation:
1
Choose a number:
89854
The number 89854 is not odd!

Process finished with exit code 0
```

Ready? Then save this file and export it as a pdf file with the name: [week2.pdf](#)

